
 


## 1) 2-Input Nor Implimentation

 

According to Calculation, worst-case delay of this Circuit is 10ns, Which can be shown in the waveform diagram.

Calculation : pMOS Delay: (5,6,7) , nMOS Delay: (3,4,5)

$$T_{01} : 2 \times (pMOS\ to1) , (nMOS\ to\ z) = 10 , 5 \\ \rightarrow WC\ Delay : 10$$

$$T_{10} : 2 \times (pMOS\ toZ) , (nMOS\ to\ 0) = 14 , 4 \\ \rightarrow WC\ Delay : 14$$

Implimentation Code :

```
`timescale 1ns/1ns



module mynor(input a,b , output w);
  wire j;
  supply0 gnd;
  supply1 vdd;
  pmos #(5,6,7)(j,vdd,a);
  pmos #(5,6,7)(w,j,b);
  nmos #(3,4,5)(w,gnd,a);
  nmos #(3,4,5)(w,gnd,b);
endmodule
```

Testbench Code :

```
`timescale 1ns/1ns

module TBNor();
  reg aa,bb;
  wire ww;
  mynor UUT(.a(aa),.b(bb),.w(ww));
  initial begin
    aa=0; bb=0;
    #100 aa=1 ; bb=0;
    #100 aa=1 ; bb=1;
    #100 aa=0 ; bb=1;
    #100 aa=0 ; bb=0;
    #100 $stop;
  end
endmodule
```

## 2) 2-to-1 Mux implementation:

 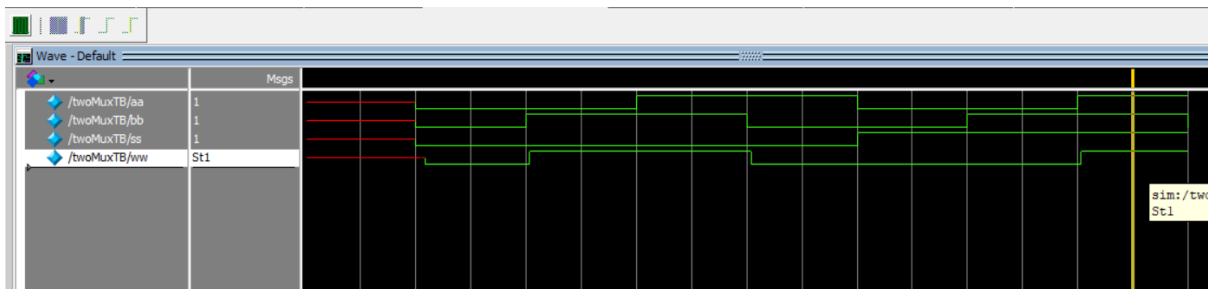

We can see through the waveform that in first half of wave form which  $S$  is 0, output just looks at  $a$  and follows it and in the second half the opposite. Which means when  $S$  is 1, output follows  $b$ .

```
`timescale 1ns/1ns
```

```
module twoOneMUX(input a,b,s , output w);
```

```
  wire j;
```

```
  supply0 gnd;
```

```
  supply1 vdd;
```

```
  nmos #(3,4,5)(w,a,s);
```

```
  pmos #(5,6,7)(j,vdd,s);
```

```
  nmos #(3,4,5)(j,gnd,s);
```

```
  nmos #(3,4,5)(w,b,j);
```

```
endmodule
```

worst case delay :

$to1 : nMOS\ toZ + pMOS\ toZ = 5 + 7 = 12$

$to0 : nMOS\ toZ + pMOS\ toZ = 5 + 7 = 12$

```
`timescale 1ns/1ns
```

```
module twoMuxTB();
```

```
  reg aa,bb,ss;
```

```
  wire ww;
```

```
  twoOneMUX UUT1(.a(aa),.b(bb),.s(ss),.w(ww));
```

```
  initial begin
```

```
    #100 ss=0; aa=0; bb=0;
```

```
    #100 ss=0; aa=0; bb=1;
```

```
    #100 ss=0; aa=1; bb=1;
```

```
    #100 ss=0; aa=1; bb=0;
```

```
    #100 ss=1; aa=0; bb=0;
```

```
    #100 ss=1; aa=0; bb=1;
```



```
    #100 ss=1; aa=1; bb=1;
```

```
    #100 ss=1; aa=1; bb=0;
```

```
  end
```

```
endmodule
```

### 3) 4-to-1 Mux

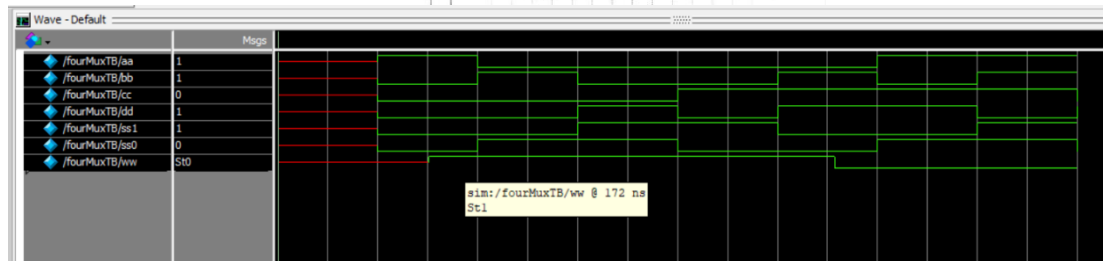 

we can see through waveform that  $s_1$  and  $s_0$  are controlling the output. When we have 00 on control we see  $a$  on output. 01 for  $b$ , 10 for  $c$  and 11 for  $d$ . ( the testbench is made in a situation that in every step the value that we expect to have it on output is different from the others so easily can be understood that circuit is working correct or not).

```
`timescale 1ns/1ns
```

```
module fourOneMUX(input a,b,c,d,s1,s0 ,
output w);
```

```
wire i,j,k,l,p;
```

```
nor #(15,21)(i,~s1,~s0,a);
```

```
nor #(15,21)(j,~s1,s0,b);
```

```
nor #(15,21)(k,s1,~s0,c);
```

```
nor #(15,21)(l,s1,s0,d);
```

```
nor #(20,28)(p,i,j,k,l);
```

```
nor #(10,14)(w,p,p);
```

```
endmodule
```

```
`timescale 1ns/1ns
```

```
module fourMuxTB();
```

```
reg aa,bb,cc,dd,ss1,ss0;
```

```
wire ww;
```

```
fourOneMUX
```

```
UUT1(.a(aa),.b(bb),.c(cc),.d(dd),.s1(ss1),.s0(ss0),.w(ww));
```

```
initial begin
```

```
#100 ss1=0; ss0=0; aa=1; bb=0; cc=0; dd=0;
```

```
#100 ss1=0; ss0=1; aa=0; bb=1; cc=0; dd=0;
```

```
#100 ss1=1; ss0=1; aa=0; bb=0; cc=0; dd=1;
```

```
#100 ss1=1; ss0=0; aa=0; bb=0; cc=1; dd=0;
```

```
#100 ss1=0; ss0=0; aa=0; bb=1; cc=1; dd=1;
```

```
#100 ss1=0; ss0=1; aa=1; bb=0; cc=1; dd=1;
```

```
#100 ss1=1; ss0=1; aa=1; bb=1; cc=1; dd=0;
```


```
#100 ss1=1; ss0=0; aa=1; bb=1; cc=0; dd=1;
```

```
end
```

```
endmodule
```

Worst Case Delay :  $15 + 20 + 2 \times 10 = 55$

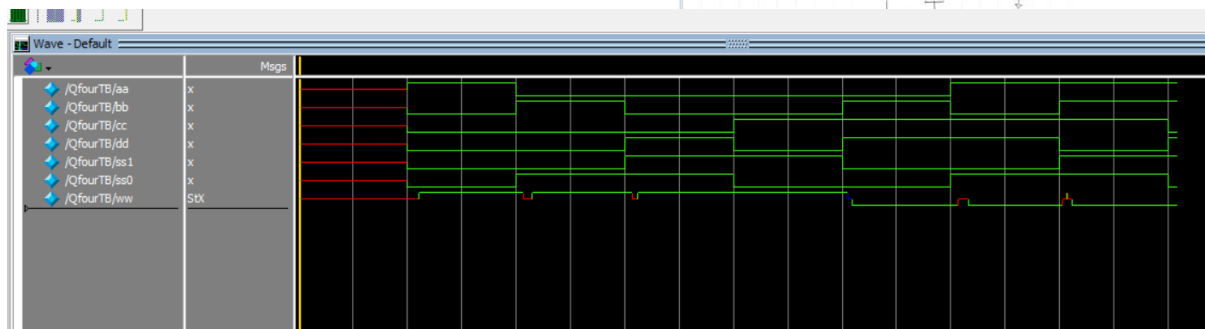Which makes sense because we have a 3-input and a four input Nor and two invertors which have been made by connecting Nors inputs together SO we expect to have a lot of Timing delay



#### 4) 4-to-1 Mux Implimenting with 2-to-1 Mux

Test bench is just like the previous question. we can see through waveform that  $s_1$  and  $s_0$  are controlling the output. When we have 00 on control we see  $a$  on output. 01 for  $b$ , 10 for  $c$  and 11 for  $d$ .

We can see that there is a lot of glitch on output comparing to the previous question but the timing delay is lower than previous one. We can examine this in next question in next question more accurate with seeing both outputs together.

```
`timescale 1ns/1ns

module QuesFourMUX(input a,b,c,d,s1,s0 , output
w);
wire i,j,s0bar , s1bar;
supply0 gnd;
supply1 vdd;
//Mux1 a,b
nmos #(3,4,5)(i,b,s0);
nmos #(3,4,5)(i,a,s0bar);
//s0 inverter
nmos #(3,4,5)(s0bar,gnd,s0);
pmos #(5,6,7)(s0bar,vdd,s0);
//Mux2 c,d
nmos #(3,4,5)(j,c,s0bar);
nmos #(3,4,5)(j,d,s0);
//Mux3
nmos #(3,4,5)(w,j,s1);
nmos #(3,4,5)(w,i,s1bar);
//s1 inverter
nmos #(3,4,5)(s1bar,gnd,s1);
pmos #(5,6,7)(s1bar,vdd,s1);
endmodule
```

```
`timescale 1ns/1ns

module fourMuxTB();
reg aa,bb,cc,dd,ss1,ss0;
wire ww;

fourOneMUX
UUT1(.a(aa),.b(bb),.c(cc),.d(dd),.s1(ss1),.s0(ss0),.w(ww));


initial begin
#100 ss1=0; ss0=0; aa=1; bb=0; cc=0; dd=0;
#100 ss1=0; ss0=1; aa=0; bb=1; cc=0; dd=0;
#100 ss1=1; ss0=1; aa=0; bb=0; cc=0; dd=1;
#100 ss1=1; ss0=0; aa=0; bb=0; cc=1; dd=0;

#100 ss1=0; ss0=0; aa=0; bb=1; cc=1; dd=1;
#100 ss1=0; ss0=1; aa=1; bb=0; cc=1; dd=1;
#100 ss1=1; ss0=1; aa=1; bb=1; cc=1; dd=0;
#100 ss1=1; ss0=0; aa=1; bb=1; cc=0; dd=1;

end

endmodule
```

# 5) Examine both 4-to-1 Muxes together

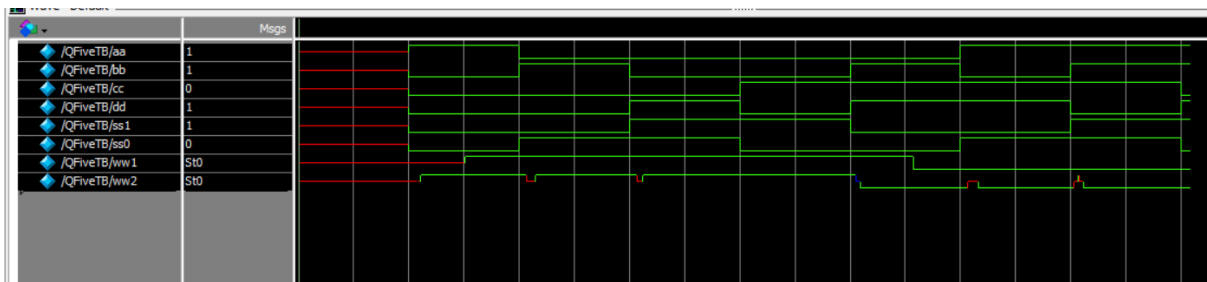

ww1 is output for Mux made with Nor Gates and ww2 is output for 4-1Mux made with 3 2-1 Muxes. As we can see delay for ww1 is much more than ww2 which is because in first circuit there are much more transistors in use ( $\cong 32$  switches) but in second circuit this number is much lower (10 Switches)

## Hand drawn waveform for Problem 1.

