

In this project we are going to design a **Divider** circuit.

```

Ln#
1  `timescale 1ns/1ns
2  module Q_reg(input clk, rst, cen, incrmnt, input [7:0] pin, output reg [7:0] pout);
10
11  module M_reg(input clk, rst, cen, input [7:0] pin, output reg [7:0] pout);
18
19  module A_reg(input clk, rst, cen, input [7:0] pin, output reg [7:0] pout);
26
27  module Mux(input [7:0] a, b, input sla, slb, output [7:0] s);
31
32  module Subtractor(input [8:0] a, b, output logic [15:0] po);
37
38  module Shifter (input [15:0] a, output [15:0] out);
41
42  module counter(input cen, iz, clk, rst, output logic [2:0] po, output co);
53
54  module counterTB ();
67
68  module DataPath(input clk, rst, ldA, ldshift, ldM, ldQ, ldSub, ldDividend, initA, initCount, countEn,
69  input [7:0] Dividend_bus, Divisor_bus, output [7:0] quationt, remainder, output countCo );
70
71  wire [2:0] count ;
72  wire [7:0] Qreg, Mreg, Areg, QBus, Abus, sub, Qshift, Ashift, mx ;
73  wire [15:0] shiftin, shiftout ;
74  Q_reg Dividend (clk, rst, ldQ, ~sub[7], QBus, Qreg);
75  M_reg Divisor (clk, rst, ldM, Divisor_bus, Mreg);
76  A_reg Afill (clk, initA, ldA, Abus, Areg);
77  Subtractor Subt ((1'b0,Areg), (1'b0,Mreg), sub);
78  Mux abus (mx, Ashift, ldSub, ldshift, Abus);
79  Mux SUB (sub, Areg, ~sub[7], sub[7], mx);
80  Mux qbus (Dividend_bus, Qshift, ldDividend, ldshift, QBus);
81  counter cnt (countEn, initCount, clk, rst, count, countCo);
82  assign shiftin = {Areg, Qreg};
83  Shifter shift (shiftin, shiftout);
84  assign {Ashift[7:0], Qshift[7:1], Qshift[0]} = {shiftout[15:1], ~sub[7]};
85
86  assign quationt = Qreg;
87  assign remainder = Areg;
88  endmodule
89

```


DataPath Codes. Assuming all modules and wiring them together in DataPath module.

```

90  module DataPathTB();
91  reg clk = 0 ;
92  reg rst, ldA, ldshift, ldM, ldSubReg, ldQ, initA, initCount, ldSub, ldDividend, countEn;
93  reg [7:0] Dividend_bus, Divisor_bus;
94  wire [7:0] quationt, remainder ;
95  DataPath UUT1 (clk, rst, ldA, ldshift, ldM, ldSubReg, ldQ, ldSub, ldDividend, initA, initCount, countEn, Dividend_bus, Divisor_bus, quationt, remainder, countCo);
96  always #100 clk = ~clk;
97  initial begin
98  Dividend_bus = 8'b00011100;
99  Divisor_bus = 8'b00000110;
100  //LOAD
101  ldA = 1 ; ldM = 1 ; ldQ = 1 ; ldshift = 1; initA = 1;
102  rst = 0 ; initCount = 1 ; ldSub = 0; ldDividend = 1; countEn = 1;
103  #150
104  //shift
105  ldA = 1 ; ldM = 0 ; ldQ = 1 ; ldshift = 1; initA = 0;
106  rst = 0 ; initCount = 0 ; ldSub = 0; ldDividend = 0; countEn = 1;
107  #150
108  //Minuse
109  ldA = 1 ; ldM = 0 ; ldQ = 1 ; ldshift = 1; initA = 0;
110  rst = 0 ; initCount = 0 ; ldSub = 1; ldDividend = 0; countEn = 1;
111
112  #150 $stop;
113  //
114  end
115  endmodule

```

 TestBench for DataPath. Assuming All control Signals that should come from controller manually just to test the Functionality of circuit.



we have not connected the Controller Unit so we don't expect Dividing from this circuit.


Hopefully DataPath is working Correctly.

```

116
117 module Controller (input clk, rst, START, countCo, output logic ldA, ldshift, ldM, ldQ, ldSub, ldDividend, initA, initCount, countEn, READY);
118     parameter Idle = 3'd0, Starting = 3'd1, Load = 3'd2, Shift = 3'd3, Minuse = 3'd4;
119     logic [2:0] ps, ns = 3'd0;
120     always @(ps, START, countCo) begin
121         {ldA, ldshift, ldM, ldQ, ldSub, ldDividend, initA, initCount, countEn, READY} = 10'b0;
122     end
123     case (ps)
124     Idle : begin ns = (START) ? Starting : Idle;
125             READY = 1; end
126     Starting : begin ns = (START) ? Starting : Load;
127             end
128     Load : begin ns = Shift;
129             {initA, ldQ, ldM, initCount, ldDividend} = 5'b11111; end
130     Shift : begin ns = Minuse;
131             {ldA, ldQ, ldshift, countEn} = 4'b1111; end
132     Minuse : begin ns = (countCo) ? Idle : Shift;
133             {ldA, ldSub} = 2'b11; end
134     default ns = 3'b0;
135     endcase
136 end
137 always @(posedge clk, posedge rst) begin
138     if (rst) ps <= 3'b000;
139     else ps <= ns;
140 end
141 endmodule
142
143 module ControllerTB();
144     logic clk = 1, rst = 0, START = 0, countCo = 0;
145     wire ldA, ldshift, ldM, ldQ, ldSub, ldDividend, initA, initCount, countEn, READY;
146     Controller UUT1 (clk, rst, START, countCo, ldA, ldshift, ldM, ldQ, ldSub, ldDividend, initA, initCount, countEn, READY);
147     always #100 clk = ~clk;
148     initial begin
149         #90 START = 1;
150         #140 START = 0;
151         #800;
152         #105 countCo = 1; START = 0;
153         #400 $stop;
154     end
155 endmodule
156


```

 Assuming All Signals that should come from DataPath as inputs manually just to test the Functionality of circuit.



Aparantly Controller is Working Correctly. In each state control signals that we want are assuming.

 
Now connecting controler to DataPath should work correctly. Hopefully!




When the READY signal is turned on, we read the outputs and they are right according to inputs.

Beautifully Done!


Quartus

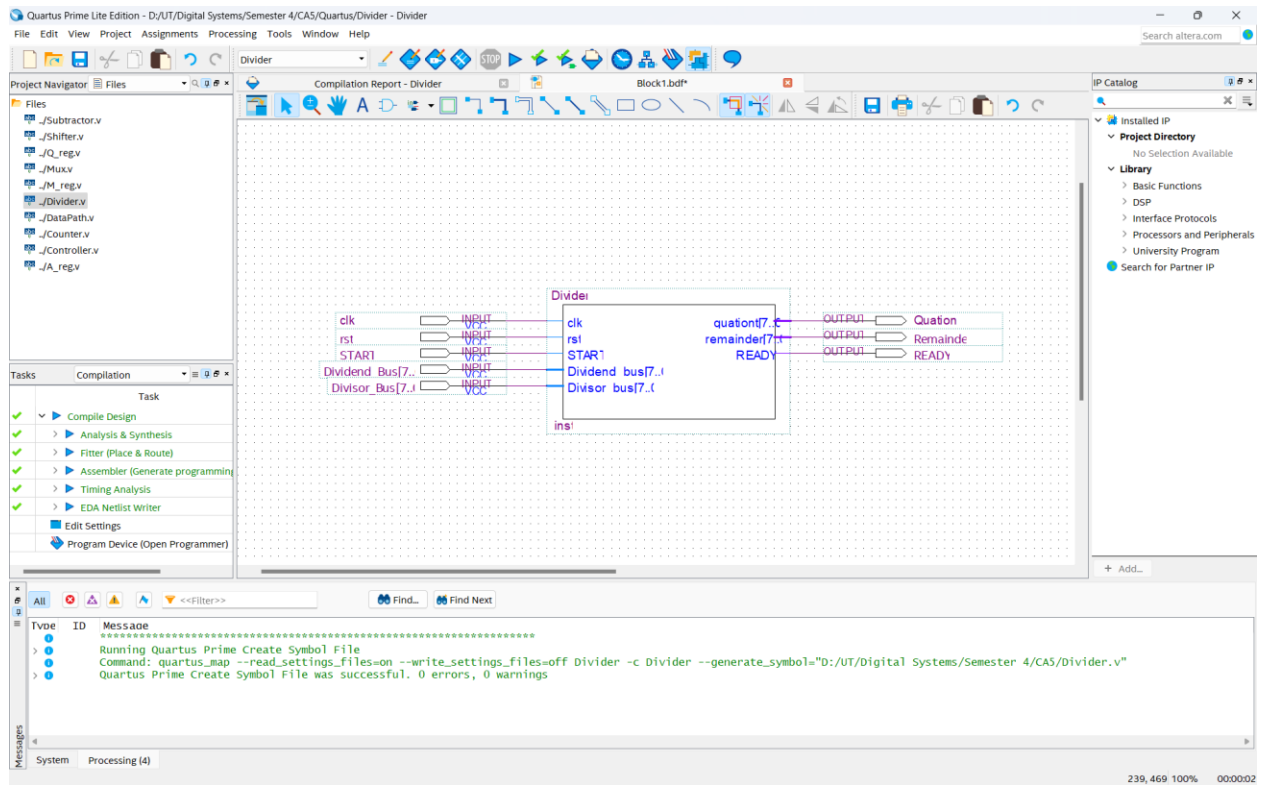

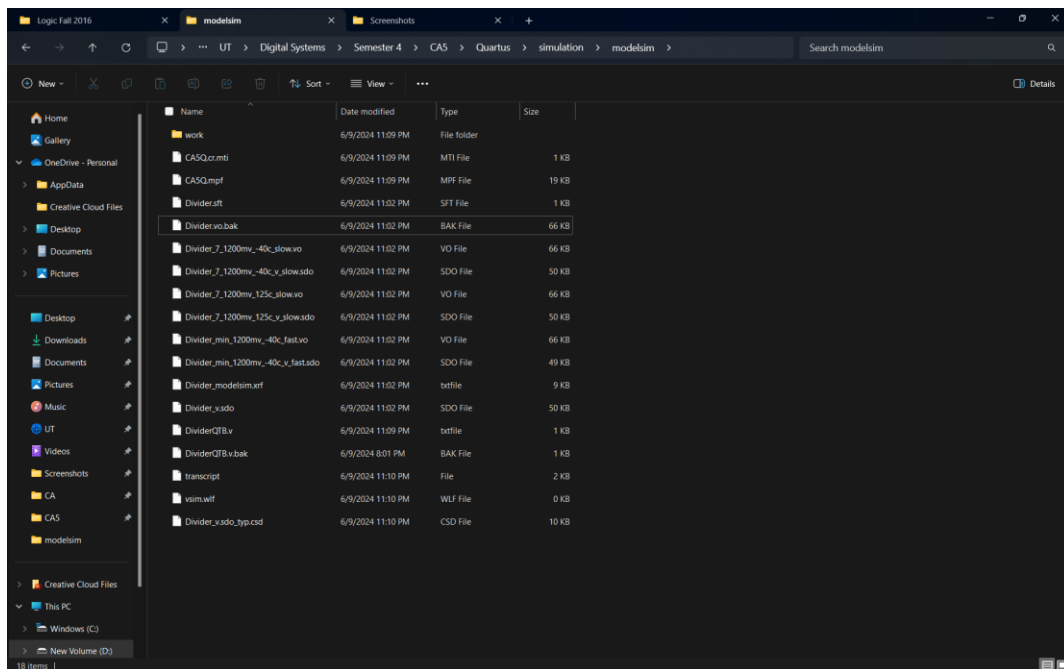
Symbol for Top level block diagram in quartus.



.sdo and .vo files are created.

 

 in this simulation we can see timing is included.



Timing is obvious in this Waveform.

